

# Math 335 Portfolio

Jean Marie Linhart

January 2019

## 1 Induction Proofs

### 1.1 Ordinary Induction

According to Kirchoff's Voltage Laws (KVL), we have the following equation:

$$\begin{aligned} -12 + V_{R_3} + 3V_F &= 0 \\ \implies V_{R_3} &= 12 - 3V_F \\ \implies R_3 &= \frac{V_{R_3}}{I_{sccR_3}} = \frac{V_{R_3}}{I_F} = \frac{12 - 3V_F}{I_F} \end{aligned}$$

- In case of  $V_F = 3V \longrightarrow 3.4V$

$$\begin{aligned} I_F &= 25mA - 30mA \\ \implies R_3 &\in \left[ \frac{12 - 3 \times 3.4}{30 \times 10^{-3}}; \frac{12 - 3 \times 3}{25 \times 10^{-3}} \right] \\ \iff R_3 &\in [60; 120](\Omega) \end{aligned}$$

- Choose  $R_1 = 40000\Omega$ , we have the following expression:

$$I_{R_2} = I_L = \frac{0.7}{40000} = 1.78 \times 10^{-6}(A)$$

Results below can be extracted by applying kirchoff's Voltage Laws.

$$\begin{aligned} -12 + V_{R_2} + V_{R_L} &= 0 \\ \implies V_{R_2} &= 12 - V_{R_L} = 12 - 0.7 = 11.3V \\ \implies R_2 &= \frac{V_{R_2}}{I_{R_2}} = 645414(\Omega) \end{aligned}$$

Base on the value of  $R_L$  measured by VOM, the following results can be infered:

$$R_2 = \frac{11.3}{\frac{0.7}{R_L}} = \frac{11.3 \times R_L}{0.7} = 12.14 R_L(\Omega)$$

Applying Kirchoff's Laws:

$$\begin{aligned}I_{R_1} &= I_{R_2} + I_{R_3} \\ \implies I_{R_1} &= I_{R_2} + I_F \\ \implies I_{R_1} &= \frac{0.7}{R_2} + I_F \\ \implies I_{R_1} &\in [0.025; 0.03](A)\end{aligned}$$

Measurement results in laboratory reportedly show that voltage at the two ends of the capacitor varies around  $12\sqrt{2}(V)$

$$V_{0C} = 12\sqrt{2}(V)$$

• In case of the worst situation when  $V_{DC} = 18.8(V)$   $R_1$  is designed in ways such that  $V_{DC} = 12(V)$

$$\begin{aligned}\implies R_1 &= \frac{18.8 - 12}{I_{R_1}} \\ \implies R_1 &\in [227; 275]\end{aligned}$$

Power: Power Index  $\geq 1.5$  In case of  $V_{DC}$  exceeds the common voltage of  $12V$ , the circuit can withstand up to  $18V$  before suffering structural damages.

$$\begin{aligned}\implies V_{DC} without R_1 &= 18\sqrt{2} \\ \implies P_{R_1} &= \frac{(18\sqrt{2} - R_1)^2}{R_1} \\ \implies R_1 &\in [227; 211]\end{aligned}$$

Procedure:

1. Components list

- Zener Diode
- $100\Omega$  Resistor
- $470000\Omega$  Resistor
- 3 LEDs
- C1815 NPN Transistor
- Light Sensing Resistor
- 4 Diodes

2.  $R_1, R_2, R_3$  Build Method

$$R_3 = R = 100(\Omega).$$