

HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY



Report Project 1: A LIGHT SENSING CIRCUIT



Lecturer:
NGUYEN TRAN HUU NGUYEN

Course:
ELECTRONIC DEVICES AND
CIRCUIT(LAB)

May 8th, 2019

GROUP MEMBERS

NAME

ID

NGO QUI THU

1652595

NGUYEN HUU GIA HUY

1652242

TRAN HOANG VIET LONG

1652350

TRUONG VAN QUANG DAT

1652142

PHAM LE THE ANH

1652026

VUONG LE HUY

1652252

Contents

Light Sensing Circuit

Group 1

May 8th, 2019

1 R_1, R_2, R_3 Calculation and Power Evaluation

1.1 R_1, R_2 and R_3 Calculation

According to Kirchoff's Voltage Laws (KVL), we have the following equation:

$$\begin{aligned} -12 + V_{R_3} + 3V_F &= 0 \\ \Rightarrow V_{R_3} &= 12 - 3V_F \\ \Rightarrow R_3 &= \frac{V_{R_3}}{I_{scR_3}} = \frac{V_{R_3}}{I_F} = \frac{12 - 3V_F}{I_F} (\Omega) \end{aligned}$$

- In case of $V_F = 3V \rightarrow 3.4V$.

$$\begin{aligned} I_F &= 25mA - 30mA \\ \Rightarrow R_3 &\in \left[\frac{12 - 3 \times 3.4}{30 \times 10^{-3}}; \frac{12 - 3 \times 3}{25 \times 10^{-3}} \right] \\ \Leftrightarrow R_3 &\in [60; 120] (\Omega) \end{aligned}$$

- Choose $R_L = 40000\Omega$, we have the following expression:

$$I_{R_2} = I_L = \frac{0.7}{40000} = 1.78 \times 10^{-6} (A)$$

Results below can be extracted by applying kirchoff's Voltage Laws.

$$\begin{aligned} -12 + V_{R_2} + V_{R_L} &= 0 \\ \Rightarrow V_{R_2} &= 12 - V_{R_L} = 12 - 0.7 = 11.3 (V) \\ \Rightarrow R_2 &= \frac{V_{R_2}}{I_{R_2}} = 645414 (\Omega) \end{aligned}$$

Base on the value of R_L measured by VOM, the following results can be inferred:

$$R_2 = \frac{11.3}{\frac{0.7}{R_L}} = \frac{11.3 \times R_L}{0.7} = 12.14 R_L (\Omega)$$

Applying Kirchoff's Laws:

$$\begin{aligned}
 I_{R_1} &= I_{R_2} + I_{R_3} \\
 \implies I_{R_1} &= I_{R_2} + I_F \\
 \implies I_{R_1} &= \frac{0.7}{R_2} + I_F \\
 \implies I_{R_1} &\in [0.025; 0.03](A)
 \end{aligned}$$

Measurement results in laboratory reportedly show that voltage at the two ends of the capacitor peaks at $12\sqrt{2}(V)$.

$$V_{0C} = 12\sqrt{2}(V)$$

• In case of the worst situation when $V_{DC} = 18.8(V)$ so that R_1 is going to be designed in a way such that $V_{DC} = 12(V)$.

$$\begin{aligned}
 \implies R_1 &= \frac{18.8 - 12}{I_{R_1}} \\
 \implies R_1 &\in [227; 275](\Omega)
 \end{aligned}$$

1.2 Power Evaluation

Given the fact that, the circuit is designed to operate normally at the 12V voltage level. While the value of V_{AC} reportedly stations at 14V ($V_{AC} = 14V$), which resulted in the following value:

$$V_{DCwithoutR_1} = 18.8(V)$$




That result leads to the below calculations:

$$\begin{aligned}
 &\bullet V_{R_1} = 18.8 - 12 = 6.8(V) \\
 &\bullet P_{R_1} = \frac{(18\sqrt{2} - R_1)^2}{R_1} \\
 \implies P_{R_1} &\in [0.168; 0.204](W)
 \end{aligned}$$

Given the Safe Factor to be ≥ 1.5 . If V_{AC} exceeds the common voltage of 12V, the circuit can withstand up to 18.8V before suffering structural damages.

$$\begin{aligned}
 P_{R_1} &= \frac{(18\sqrt{2} - 12)^2}{R_1} \\
 \implies P_{R_1} &\in [0.7; 0.8](W)
 \end{aligned}$$

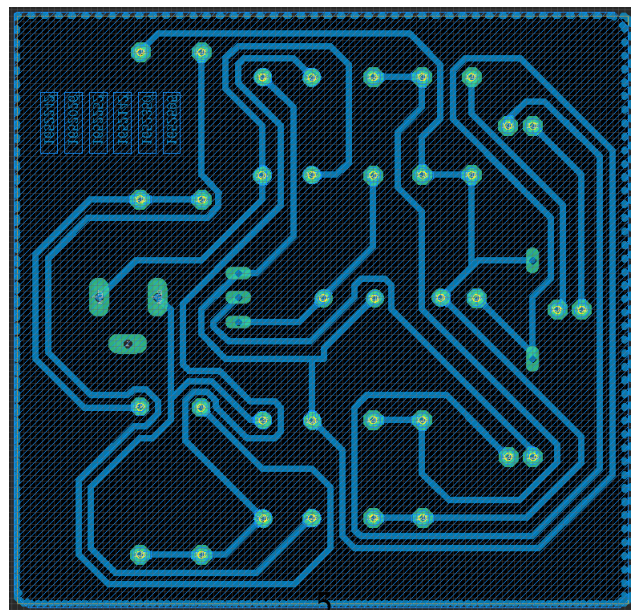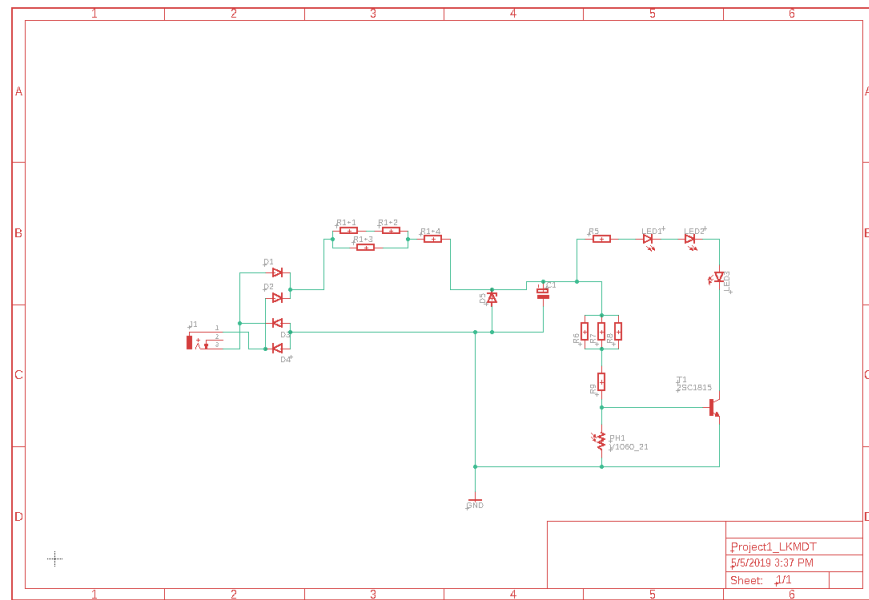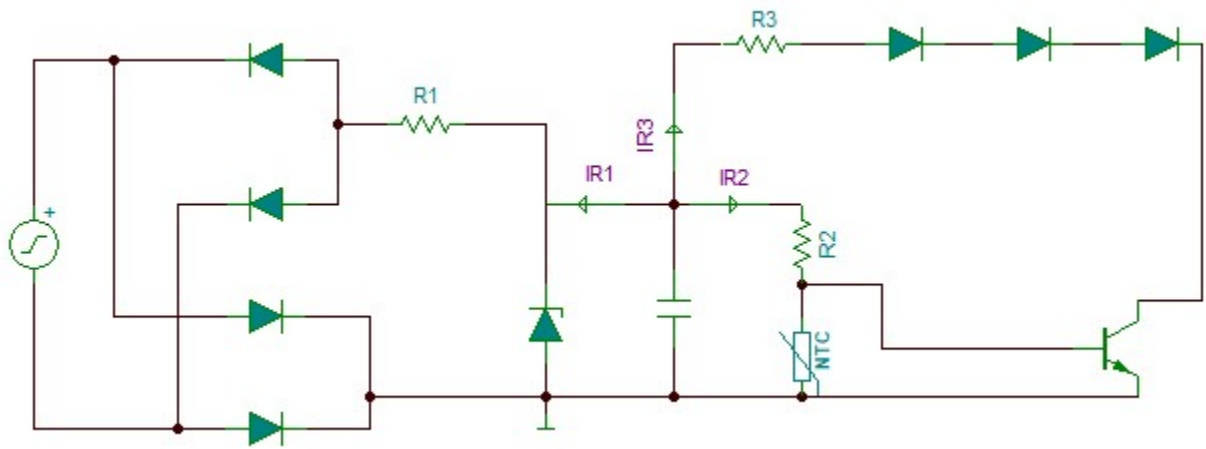• Choose $R_1 = 250\Omega, 0.5W$ in order to guarantee that the circuit can withstand the voltage up to 1.5 times higher than the normal designed voltage.



2 Proceeding Steps

2.1 Components List

- 100Ω , $1/4W$ Resistor
- 150Ω , $0.5W$ Resistor
- $470K\Omega$, $1/4W$ Resistor
- Light Sensing Resistor
- Zener Diode
- C1815 NPN Transistor
- 3 LEDs
- 4 Diodes

2.2 R_1, R_2, R_3 Build Method

2.2.1 R_1 Component

Only 150Ω , $0.5W$ Resistor is available. Thus system of R_1 resistors are built as follow in order to get the exactly calculated value $R_1 = 250(\Omega)$.


R1:



2.2.2 R_2 Component

System of R_2 resistors are built as follow in order to get the exactly calculated value $R_2 = 645(K\Omega)$.

R2:

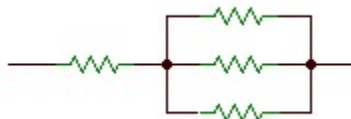

2.2.3 R_3 Component

$$R_3 = R = 100(\Omega).$$

R3:

