

# HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY



---

## Report Project 1: A LIGHT SENSING CIRCUIT

---



*Lecturer:*  
NGUYEN TRAN HUU NGUYEN

*Course:*  
ELECTRONIC DEVICES AND  
CIRCUIT(LAB)

May 8<sup>th</sup>, 2019

# GROUP MEMBERS

*NAME*

*ID*

NGO QUI THU

1652595

NGUYEN HUU GIA HUY

1652242

TRAN HOANG VIET LONG

1652350

TRUONG VAN QUANG DAT

1652142

PHAM LE THE ANH

1652026

VUONG LE HUY

1652252

# Contents

<b>1</b>	<b><math>R_1, R_2, R_3</math> Calculation and Power Evaluation</b>	<b>3</b>
1.1	$R_1, R_2$ and $R_3$ Calculation . . . . .	3
1.2	Power Evaluation . . . . .	4
<b>2</b>	<b>Proceeding Steps</b>	<b>5</b>
2.1	Components List . . . . .	5
2.2	$R_1, R_2, R_3$ Build Method . . . . .	5
2.2.1	$R_1$ Component . . . . .	5
2.2.2	$R_2$ Component . . . . .	5
2.2.3	$R_3$ Component . . . . .	5

# Light Sensing Circuit

Group 1

May 8<sup>th</sup>, 2019

## 1 $R_1, R_2, R_3$ Calculation and Power Evaluation

### 1.1 $R_1, R_2$ and $R_3$ Calculation

According to Kirchoff's Voltage Laws (KVL), we have the following equation:

$$\begin{aligned} -12 + V_{R_3} + 3V_F &= 0 \\ \Rightarrow V_{R_3} &= 12 - 3V_F \\ \Rightarrow R_3 &= \frac{V_{R_3}}{I_{scR_3}} = \frac{V_{R_3}}{I_F} = \frac{12 - 3V_F}{I_F} (\Omega) \end{aligned}$$

- In case of  $V_F = 3V \rightarrow 3.4V$ .

$$\begin{aligned} I_F &= 25mA - 30mA \\ \Rightarrow R_3 &\in \left[ \frac{12 - 3 \times 3.4}{30 \times 10^{-3}}; \frac{12 - 3 \times 3}{25 \times 10^{-3}} \right] \\ \Leftrightarrow R_3 &\in [60; 120] (\Omega) \end{aligned}$$

- Choose  $R_L = 40000\Omega$ , we have the following expression:

$$I_{R_2} = I_L = \frac{0.7}{40000} = 1.78 \times 10^{-6} (A)$$

Results below can be extracted by applying kirchoff's Voltage Laws.

$$\begin{aligned} -12 + V_{R_2} + V_{R_L} &= 0 \\ \Rightarrow V_{R_2} &= 12 - V_{R_L} = 12 - 0.7 = 11.3 (V) \\ \Rightarrow R_2 &= \frac{V_{R_2}}{I_{R_2}} = 645414 (\Omega) \end{aligned}$$

Base on the value of  $R_L$  measured by VOM, the following results can be inferred:

$$R_2 = \frac{11.3}{\frac{0.7}{R_L}} = \frac{11.3 \times R_L}{0.7} = 12.14 R_L (\Omega)$$

Applying Kirchoff's Laws:

$$\begin{aligned}
 I_{R_1} &= I_{R_2} + I_{R_3} \\
 \implies I_{R_1} &= I_{R_2} + I_F \\
 \implies I_{R_1} &= \frac{0.7}{R_2} + I_F \\
 \implies I_{R_1} &\in [0.025; 0.03](A)
 \end{aligned}$$

Measurement results in laboratory reportedly show that voltage at the two ends of the capacitor peaks at  $12\sqrt{2}(V)$ .

$$V_{0C} = 12\sqrt{2}(V)$$

• In case of the worst situation when  $V_{DC} = 18.8(V)$  so that  $R_1$  is going to be designed in a way such that  $V_{DC} = 12(V)$ .

$$\begin{aligned}
 \implies R_1 &= \frac{18.8 - 12}{I_{R_1}} \\
 \implies R_1 &\in [227; 275](\Omega)
 \end{aligned}$$

## 1.2 Power Evaluation

Given the fact that, the circuit is designed to operate normally at the 12V voltage level. While the value of  $V_{AC}$  reportedly stations at 14V ( $V_{AC} = 14V$ ), which resulted in the following value:

$$V_{DCwithoutR_1} = 18.8(V)$$

That result leads to the below calculations:

$$\begin{aligned}
 \bullet V_{R_1} &= 18.8 - 12 = 6.8(V) \\
 \bullet P_{R_1} &= \frac{(18\sqrt{2} - R_1)^2}{R_1} \\
 \implies P_{R_1} &\in [0.168; 0.204](W)
 \end{aligned}$$

Given the Safe Factor to be  $\geq 1.5$ . If  $V_{AC}$  exceeds the common voltage of 12V, the circuit can withstand up to 18.8V before suffering structural damages.

$$\begin{aligned}
 P_{R_1} &= \frac{(18\sqrt{2} - 12)^2}{R_1} \\
 \implies P_{R_1} &\in [0.7; 0.8](W)
 \end{aligned}$$

• Choose  $R_1 = 250\Omega, 0.5W$  in order to guarantee that the circuit can withstand the voltage up to 1.5 times higher than the normal designed voltage.

## 2 Proceeding Steps

### 2.1 Components List

- $100\Omega$ ,  $1/4W$  Resistor
- $150\Omega$ ,  $0.5W$  Resistor
- $470K\Omega$ ,  $1/4W$  Resistor
- Light Sensing Resistor
- Zener Diode
- C1815 NPN Transistor
- 3 LEDs
- 4 Diodes

### 2.2 $R_1, R_2, R_3$ Build Method

#### 2.2.1 $R_1$ Component

Only  $150\Omega$ ,  $0.5W$  Resistor is available. Thus system of  $R_1$  resistors are built as follow in order to get the exactly calculated value  $R_1 = 250(\Omega)$ .

#### 2.2.2 $R_2$ Component

System of  $R_2$  resistors are built as follow in order to get the exactly calculated value  $R_2 = 645(K\Omega)$ .

#### 2.2.3 $R_3$ Component

$$R_3 = R = 100(\Omega).$$