

# HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY



---

## Report Project 2: A CLAP-SWITCH CIRCUIT

---



*Lecturer:*  
NGUYEN TRAN HUU NGUYEN

*Course:*  
ELECTRONIC DEVICES AND  
CIRCUIT(LAB)

May 8<sup>th</sup>, 2019

# GROUP MEMBERS

*NAME*

*ID*

NGO QUI THU

1652595

NGUYEN HUU GIA HUY

1652242

TRAN HOANG VIET LONG

1652350

TRUONG VAN QUANG DAT

1652142

PHAM LE THE ANH

1652026

VUONG LE HUY

1652252

# Contents

<b>1</b>	<b>Proceeding Steps</b>	<b>3</b>
<b>2</b>	<b>Results Evaluation</b>	<b>6</b>
<b>3</b>	<b>Application</b>	<b>6</b>

# Light Sensing Circuit

Group 1

May 8<sup>th</sup>, 2019

## 1 Proceeding Steps

- Circuit Analysis When System In Stand By State (No Sound Detected).

$$V_{G1} = 0(V)$$

Applying Kirchhoff's Voltage Law, this expression can be inferred:

$$V_{R_{4,5}} = \frac{V_1 \cdot R_5}{R_4 + R_5} = \frac{12 \times 10}{10 + 10}(V)$$

- Hence  $V_2$  and  $V_3$  share a common input value of 6 volts, the output signal of Op-Amplifier is zero.

$$\begin{aligned} V_3 &= V_2 = 6(V) \\ \implies V_{2,3} &= 0(V) \end{aligned}$$

- Thus  $V_{out}$  takes the same value with  $V_{R_1}$  and  $V_{R_2}$ .

$$V_{out} = V_{R_1} = V_{R_2} = 6(V)$$

- Circuit Analysis When System In Operation State (Clapping-Sound Is Recorded).

$$V_{G1} \neq 0(V)$$

- If a sound is recorded. The microphone converts physical sound waves into electronic pulses. Electronic signals run through wires to  $C_1$  capacitor.  $C_1$  is responsible for stabilizing the pulses.

This results in changes of  $V_{mic}$ :

$$V_{mic} = 6 - V_{G1}(V)$$

Electronically, a current would run through the circuit.

$$i = \frac{V_{mic}}{R_2} = \frac{V_{mic}}{1K(\Omega)}(A)$$

Subsequently,  $V_{out}$  suffers a voltage drop down.

$$V_{out} = 6(V) - \frac{100K(\Omega).V_{G1}}{1K(\Omega)}(V)$$

• Theoretically, Amplification at the output port  $U_1$  is demonstrated in the expression below:

$$U_1 = \frac{R_3}{R_2}(V)$$

Applying Nodal Analysis,  $V_{ref}$  can be calculated by the following formular:

$$V_{ref} = \frac{R_6}{R_6 + R_7}$$

Similarly, through Nodal Analysis,  $V_{rec}$  estimation is illustrated bellow:

$$V_{Rec} = V_{out} - 0.7(V)$$

This results in  $V_{rec} > V_{ref}$  which cause reversed polarity in the second amplifier.

$$U_2 = 0(V)$$

• Which means no electronic signal comes to Switch port.




$$V_{sw} = 0(V)$$

Meanwhile, the subsequent voltage differentiation at the two ends of LED1 makes it glow.

• Hence  $V_{sw}$  is connected to signal pin of IC 4017 counter so that  $Y_1$  would be shifted to HIGH.

In the meantime  $Y_1$  triggers the collector pin of the C1815 NPN transistor C1815. At this point, a connection is established so that a current running through the coil is generated.

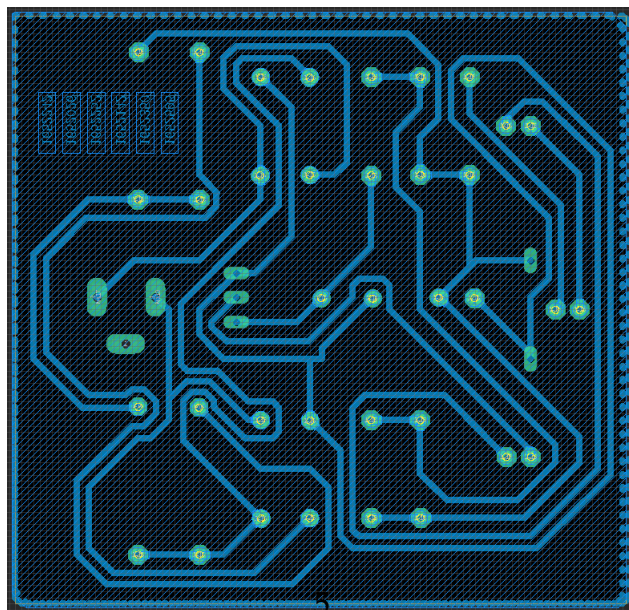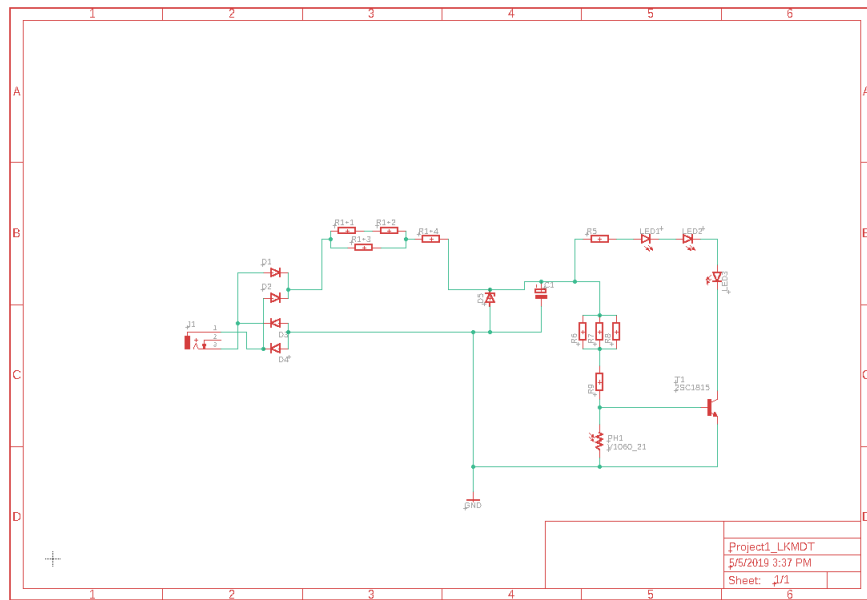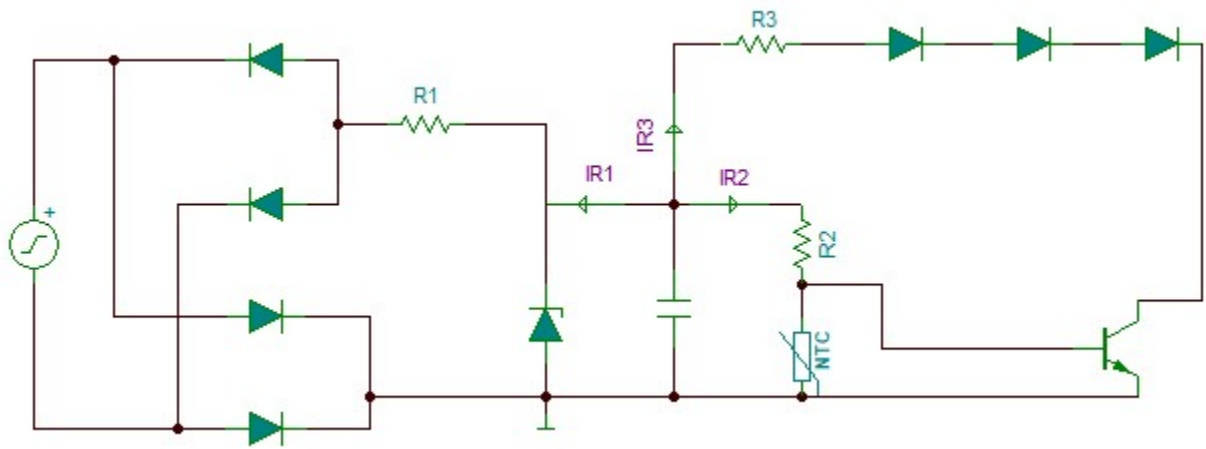Magnetic field of the coil attracts the switch conducting to connection between COM (Communication port) and NC (Normally closed port) which signals control of the device.



## 2 Results Evaluation

- ▷ Amplification:  $\times 100$ .
- ▷ Clapping range: 0.5(m).

## 3 Application

In spite of poor performance and improper functionality in noisy environment, the system performed flawlessly in quiet environment this could be attributed to the reason why clapping-switch system could be extensively used in controlling home devices (lights, heating and air-conditioning systems, fans, etc).

Nonetheless, more advanced, the system could be used as a cheap and economic their detecting system which functions as an ear listen to unidentified sound.

However longer clapping range and more precise sound detection must be taken into account in order to make the system more user-friendly commercializable.